

## CS1026 Tutorial 3

Using a decoder and external gates, design and draw the combinational circuit defined by the following three Boolean functions

$$F_1 = x'yz' + xz$$

$$F_2 = xy'z' + x'y$$

$$F_3 = x'y'z' + xy$$