

# CS1026 Lab 1

## AND GATE

(A) Design, build and test a circuit to experimentally determine the truth table of a 7411 3 Input AND gate

1 x 7411 ( Triple 3-Input AND Gate )

1 x LED

Resistors and Switches