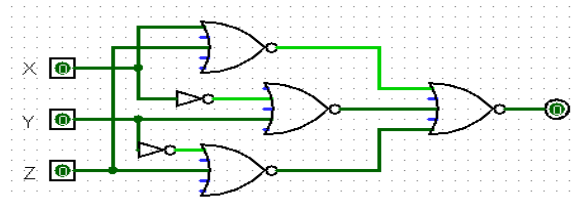


LAB 1 WRITE UP

Title: CS1026 Lab 2 (NOR Gates)**Date:** 26/10/2017**Aim:** To design a circuit to implement $F = (X + Z)(Y + Z)(X + Y + Z)$ using only NOR Gates and inverters.**Logic Diagram:****Analysis:**

- I began by finding the complement of the original function F .
- Then, using DeMorgans Theorem I expanded the function to create a function containing 3 NOR's.
- Using various Boolean Algebra Simplification theorems I then further expanded and simplified out the function until I reached a solution in the end with a single variable.
- Following this I then built and tested the circuit using Logisim to see if it was giving the desired output when the variable Z was set to 1.

Boolean Algebra:

$$F = (x+z)(y'+z)(x'+y+z)$$

$$F' = (x+z)' + (y'+z)' + (x'+y+z)'$$

$$F = [(x+z)' + (y'+z)' + (x'+y+z)']' \text{ DeMorgans}$$

$$F = [(x+z)' \cdot (y'+z)' \cdot (x'+y+z)']'$$

$$F = (x'zy' + x'z + yxz + yz + zyx' + zxy' + zx + zy' + z) \text{ Expanding}$$

$$F = z(x'y' + xy' + x' + x + y' + y + x'y + xy' + z) \text{ Simplification}$$

$$F = z(z)$$

$$F = z$$