

## CS1026 Lab 2

Design, build and test a circuit that implements a two input Exclusive or gate using only a 7400 (quad two input NAND gate) and resistors, switches and an LED.

1 x 7400 ( Quad 2 input Nand Gate )

1 x LED

Resistors and Switches

Data sheets are on course web page