

# CS1026 – Digital Logic Design

## More Synchronous Logic

Alistair Morris <sup>1</sup>

<sup>1</sup>Distributed Systems Group  
Trinity College Dublin

March 22, 2016

# Today's Overview

- 1 One more example
- 2 How fast can we go
- 3 Adding an Enable


# Classical Design Revisted [Nelson et al., 1995] I

## Example Style Question

Design a synchronous sequential circuit called *Div-by-3* having an output  $Z$  that divides the system clock frequency  $f$  CLK by 3.

- Use an output duty cycle of two-thirds
  - 2 CLK cycle high, 1 cycle low
- Design the circuit using positive-edge-triggered flip-flops
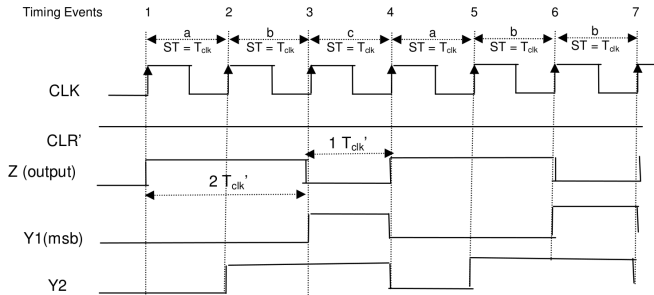
# Classical Design Revisted [Nelson et al., 1995] II



Step 1: Start with a timing diagram

# Classical Design Revisted [Nelson et al., 1995] III

Step 2: Determine the number of flip-flop based on the number of State

- No. states = 3  $\leq$  2
- Assuming Full Coding

# Classical Design Revisted [Nelson et al., 1995] IV

Step 3: Assign a unique code to each state

- A – 00
- B – 01
- C – 10

# Classical Design Revisted [Nelson et al., 1995] V

Step 4: Write the excitation-input equations

Y1Y2	Y1 <sup>+</sup>	Y2 <sup>+</sup>	Z
00	0	1	1
01	1	1	1
11	0	0	0
10	-	-	-

$$D1 = Y1+ = Y1' \cdot Y2$$

$$D2 = Y2+ = Y1'$$

$$Z = Y1'$$

10 State is never reached.

"-" means don't care

- The D flip flop excitation equation:  $D = Y+$

# Classical Design Revisted [Nelson et al., 1995] VI


More step 4..

- We need the composite K-map for each of the desired outputs:  $Y1$ ,  $Y2$ ,  $Z$



# Classical Design Revisted [Nelson et al., 1995] VII

## Step 5: Draw the Circuit Schematic

 

- We skip steps 6 and 7..
  - But you should do this in the lab/exam!

# Classical Design Revisted [Nelson et al., 1995] VIII


## The Last Lab

Design a synchronous sequential circuit identical to the previous example, except implement the design using JK flip-flops instead of D flip-flops

# Determining the Maximum Clock I

The maximum clock frequency that a system can handle is driven by the set-up, hold and margin times required by the flip flops in the synchronous system.

# Determining the Maximum Clock II

 

We can see that the clock frequency becomes limited by:

$$f_{max} = 1/T_{CLK(min)}$$

# Determining the Maximum Clock III

$T_{CLK(min)} = t_{pff(max)} + t_{pcomb(max)} + t_{h(marg)} + t_{su} + t_h$  where:


- $t_{pff(max)}$  – Maximum propagation delay time through flip-flop from the clock tick to Q output
- $t_{pcomb(max)}$  – Maximum propagation delay time through combinational logic
- $t_{h(marg)}$  – Margin time, it is always a good design practice to allow for tolerances.
- $t_{su}$  – Set-up time requirement
- $t_h$  – Hold time requirement

# Determining the Maximum Clock IV

## An Example

Determine the absolute maximum clock frequency for the divide-by-3 synchronous machine

# Determining the Maximum Clock V

 

Remember the Schematic!

# Determining the Maximum Clock VI

Going through the ICs:

- 74LS08 AND gate
  - $t_{pcomb}$  : Min at 3 ns and Max. at 18 ns
- 75LS175 D-flip-flop
  - $t_{pff}$ : Min at 0 ns and Max. at 42 ns
  - $t_{su}$ : Min at 20 ns
  - $t_h$ : Min at 0 ns



# Determining the Maximum Clock VII

So let's find the fastest clock speed:

- $T_{CLK(min)} = t_{pff(max)} + t_{pcomb(max)} + t_{h(marg)} + t_{su} = 42 + 18 + 0 + 20 = 80 \text{ ns}$
- $T_{CLK(max)} = 1/T_{CLK(min)} = 1/80 \times 10^{-9} = 12.5 \text{ MHz}$

How does this compare?

- $12.5 \text{ MHz} \implies \text{Slow}$ 
  - In comparison to modern tech

# Using Enables I


Used to stop the count at times and then continue counting

- Basis of *Full-Encoded Stoppable Counter*
  - Counter will count up as long as EN high
  - Else STOP counting
 
# Using Enables II

State Diagram for a three-bit ( $Y1, Y2, Y3$ )

- Also called a *Full-Encoded Stoppable Counter*



# Using Enables III

Composite K-map for a 3-bit binary up stoppable counter with:

- Enable input EN
- Asynchronous clear input CLR
- Ripple-carry out RCO.

$Y_1Y_2Y_3$										
EN		000	001	011	010	100	101	111	110	
0		000	001	011	010	100	101	111	110	} $Y_1^+ Y_2^+ Y_3^+$
1		001	010	100	011	101	110	000	111	
		0 0 0 0				0 0 1 0				} RCO

Note: CLR=1  $\rightarrow Y_1Y_2Y_3 = 000$


## Using Enables IV

We derive the flip-flop input excitation equation and RCO output equation from the composite K-map or (need 3 flip-flops):

- $D1 = Y1^+ = EN.Y1'.Y2.Y3 + Y1.Y2' + Y1.Y3' + EN'.Y1$
- $D2 = Y2^+ = EN.Y2'.Y3 + Y2.Y3' + EN'.Y2$
- $D3 = Y3^+ = EN.Y3' + EN'.Y3$
- $RCO = Y1.Y2.Y3$

 
## Using Enables V

In order to maintain the benefits of a synchronous system (avoiding clock glitches), it is important that the clock to all of the components remains the same.



■ I.E. NOT TO DO THIS!

# Using Enables VI

 

Instead, if you need to enable a flip-flop, use one with enable capability designed in or use the MUX as shown

# Using Enables VII

Moral of the story:

- Flip-flops with enable allows the designers to focus on input/output sync
- Enabled flip-flops simply require a connection to the enable pin



# References (Homework) I



Nelson, V. P., Nagle, H. T., Carroll, B. D., and Irwin, J. D.  
(1995).

*Digital logic circuit analysis and design.*

Prentice-Hall, Inc.