

Lab 2

Shane Sheehan
sheehas1@scss.tcd.ie

Semester II (2017)

1 POS function using NOR gates only

- Implement: $F = (X + Z)(Y' + Z)(X' + Y + Z)$
 - Hint: Start by complementing inputs of the AND gate