

CS1026 – Digital Logic Design

Feedback Circuits

Alistair Morris ¹

¹Distributed Systems Group
Trinity College Dublin

March 7, 2016

Today's Overview

- 1 Introduction
- 2 SR Flip FLops
- 3 Async Issues
- 4 Circuit Analysis

A quick recap.. I


Last time we looked at a *SR Latch*:

- A multivibrator
- Used to store an input value

Real World Use

Often we want to react to what *has* happened

The SR Flip Flop [Kojima, 2013] I

 

Set and **R**eset inputs

The SR Flip Flop [Kojima, 2013] II

Q^+ defines the next output state (Q_{next})

- Q^+ dependent on:
 - Inputs S and R
 - Current state: Q

The SR Flip Flop [Kojima, 2013] III

Characteristic Table				Excitation Table			
S	R	Q_{next}	Action	Q	Q_{next}	S	R
0	0	Q	Hold State	0	0	0	X
0	1	1	Reset	0	1	1	0
1	0	1	Set	1	0	0	1
1	1	X	Now allowed	1	1	X	0

Table: Characteristic and Excitation Table

You can think of this as the sequential circuit equivalent to a combination circuit's truth table

The SR Flip Flop [Kojima, 2013] IV

S	R	Q^+
0	0	Q
1	0	1
1	1	X

If we feel lazy:

- Write down the *Compressed Characteristic Table*
- We almost have a truth table

The SR Flip Flop [Kojima, 2013] V

		Q	
		0	1
SR	00	<u>0</u>	<u>1</u>
	01	<u>0</u>	0
	11	<u>0</u>	0
	10	1	<u>1</u>

We can also do a K-Map

- But remember states (mid-terms) 3, 4 and 7
 - These define unstable states (i.e. don't go there)
 - Δ time needed for flip flop to respond

The SR Flip Flop [Kojima, 2013] VI

		Q	
		0	1
SR	00	<u>0</u>	<u>1</u>
	01	<u>0</u>	0
	11	<u>0</u>	0
	10	1	<u>1</u>

The K-Map works too!

■ $Q^+(S, R, Q) = QR' + SR'$

SR Flip-Flop Issues I

SR Flip Flop denotes a *Latch*:

- No Clock to sync signals
 - \therefore We have an async circuit

SR Flip-Flop Issues II

This becomes problematic in circuit design:

- A *race condition* exists:

- $\{S, R, Q\} = 0$

- $S \implies 1 \implies \{S, R, Q\} = 100$ (Unstable state!!) \implies
 $Q^+ = 1 \implies \{S, R, Q\} = 101$

- After ΔT

SR Flip-Flop Issues III

If the S and R inputs change quickly before the output settles into a new stable state:

- The input provides a race condition
- Each trying to change the output first). If the output becomes a predictable stable state
 - then we have a non-critical race

SR Flip-Flop Issues IV

A critical race occurs if the circuit output ends in an *unpredictable* stable state.

- For Example

- $S, R, Q = 110$

- SR becomes 00

- S changes first – $\{S, R, Q\} = 010 \implies Q^+ = 0$

- R changes first – $\{S, R, Q\} = 100 \implies Q^+ = 1$

SR Flip-Flop Issues V

SR \ Q	0	1
	0	1
00	<u>0</u>	<u>1</u>
01	<u>0</u>	0
11	<u>0</u>	0
10	1	<u>1</u>

Note that depending on if S changed first or R changed first:

- Final state will be different
- This means we have a critical race.

Finite State Machines I

Step 1. Write the Compressed Characteristic Table

S	R	Q+
0	0	Q
0	1	0
1	0	1
1	1	0

(reset dominant)




Step 2. Present State /Next State (PS/NS) Table

S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0



 Step 3. Draw a circle for each state (one output, Q, so 2-state)
Step 4. Draw arrow showing change for each possible input in each state.



We can draw the relation between states in the SR Flip Flop

Finite State Machines II

A completely specified state machine is one for which all input conditions specify each next state condition:

- $\sum = 1$ Rule
- For state 0 in SR Flip Flop:
 - $(S' + R) + SR' = 1$

Finite State Machines III

Step 1. Write the Compressed Characteristic Table

S	R	Q+
0	0	Q
0	1	0
1	0	1
1	1	0

(reset dominant)




Step 2. Present State /Next State (PS/NS) Table

S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0



Step 3. Draw a circle for each state (one output, Q, so 2-state)

 
Step 4. Draw arrow showing change for each possible input in each state.



In the case of incomplete state machines:

- We can consider those states as *don't cares*

Finite State Machines IV

 

Algorithmic State Machine (ASM) help us out even more!

- Basically a *Flowchart*

Finite State Machines V

Chart uses three symbols:

- Rectangle – State Box
- Diamond – Decision Box
 - If true take “1” path
 - Else take “0” path
- Oval – Output box

References (Homework) I



Kojima, S. (2013).

Sr flip-flop.

US Patent 8,497,722.