

Lab 6

Shane Sheehan
sheehas1@scss.tcd.ie

Semester II (2017)

1 More Flip Flops

- Design a *negatively* edge triggered D Flip flops
- Give the Present-State/Next-State (PS/NS) Table for a JK Flip Flop
- Give the Algorithmic State Machine (ASM) for a JK Flip Flop