

# CS1026 – Digital Logic Design

## Sequential Logic Analysis

Shane Sheehan <sup>1</sup>


<sup>1</sup>ADAPT  
Trinity College Dublin

February 20, 2017

# Today's Overview

- 1 Method of analysing sync circuits
- 2 Applying the five step analysis technique
- 3 A useful book

 
## Analysing Sync Circuits [Nelson et al., 1995] I



We can use Flip Flops to work out how a Synchronous circuit works

- How does it behave?
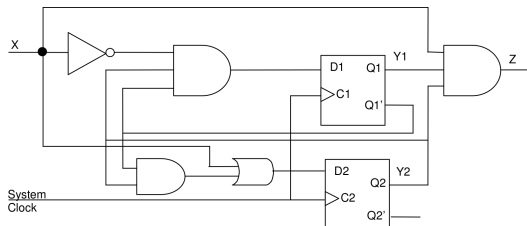
# Analysing Sync Circuits [Nelson et al., 1995] II



Assign a present state variable to each flip flop in the system.


- $Y_i$  represents flip-flop outputs for  $i = 1, 2, 3, \dots$

# Analysing Sync Circuits [Nelson et al., 1995] III

Write the excitation-input equation for each of the flip-flops and the external-output (Moore and/or mealy equations).

- After completing this step, we define  $D_i$ ,  $J_i$ ,  $K_i$ ,  $T_i$  where  $i = 1, 2, 3 \dots$ 
  - This denotes the number of flip-flops used

 
# Analysing Sync Circuits [Nelson et al., 1995] IV



Substitute the excitation input equation into the characteristic equations of the flip-flops.

- This obtains the “next state” equations

 
# Analysing Sync Circuits [Nelson et al., 1995] V



For D flip-flops:

- $Y_i = D_i$  for  $i = 1, 2, 3, \dots$
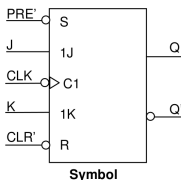
# Analysing Sync Circuits [Nelson et al., 1995] VI



**Characteristic Table**

J	K	Q <sup>+</sup>	Comment
0	0	Q	no change
0	1	0	reset condition
1	0	1	set condition
1	1	Q'	toggle


**Characteristic equation:**  $Q^+ = J \cdot Q' + K' \cdot Q$

For J-K flip-flops:

■  $Y_i = J_i \cdot Y_i' + K_i' \cdot Y_i$  for  $i = 1, 2, 3, \dots$


 
# Analysing Sync Circuits [Nelson et al., 1995] VII



**Characteristic Table**

T	Q*	Comment
0	Q	no Change
1	Q'	toggle

**Characteristic equation:**  $Q^* = T'.Q + T.Q'$

Also for T flip-flops

■  $Y_i = T_i \oplus Y_i$  for  $i = 1, 2, 3, \dots$

but we don't see these much now!

# Analysing Sync Circuits [Nelson et al., 1995] VIII

Y1	Y2	X	Y1 <sup>+</sup>	Y2 <sup>+</sup>	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Obtain a Present State (PS) /Next State (NS) table (or a composite K-map) using the next state and external-out equations

- Separate K-maps can be used for the external outputs!


# Analysing Sync Circuits [Nelson et al., 1995] IX

Y1	Y2	X	Y1 <sup>+</sup>	Y2 <sup>+</sup>	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1


Use the PS/NS table or the K-map to obtain a state diagram

- Then we can draw ASM chart or timing diagram to show the behavior of the circuit

# An example I

 


## An example II

 

Note: We have a Mealy-type machine since the output depends on external input and flip-flop outputs.

## An example III

 

Assign a present state variable to each flip flop in the synchronous system.  $Y_i$  representing flip-flop outputs for  $i = 1, 2, 3, \dots$

### Hint

Refer to the schematic!

## An example IV

Write the excitation-input equation for the flip-flops and the equation for the external-output (Moore and/or mealy equations). After this step is completed, the values of  $D_i$ ,  $Z$  should be defined for all flip-flops:

- $D1 = X'.Y1'.Y2$
- $D2 = Y1'.Y2 + X$
- $Z = Y1.Y2.X$

# An example V

Substitute the excitation-input equation into the characteristic equations for the flip-flops to obtain the *next state* equations.

- Remember for D flip-flops:

- $Y_i = D_i$  for  $i = 1, 2, 3, \dots$
- $Y1 = D1 = X'.Y1'.Y2$
- $Y2 = D2 = Y1'.Y2 + X$



# An example VI

PS/NS Table

Y1	Y2	X	Y1 <sup>+</sup>	Y2 <sup>+</sup>	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

OR

Composite K-map where:


→ Ys and Xs are independent variables

→ Ys<sup>+</sup> and Zs are Dependent

		X	
		0	1
Y <sub>1</sub> Y <sub>2</sub>	00	00,0	01,0
	01	11,0	01,0
	11	00,0	01,1
	10	00,0	01,0
		Y <sub>1</sub> <sup>+</sup> Y <sub>2</sub> <sup>+</sup> . Z	

Obtain a PS/NS table or a composite K-map using the next state and external-output (Mealy and/or Moore) equations. Separate K-maps can also help with the external outputs.


# An example VII

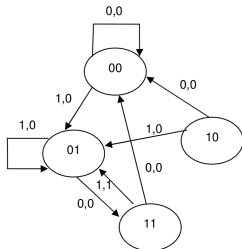

Classic State machine

- \* Links show input, output in 1s and 0s
- \* State is inside the circles

## Legend

 


## Notes

- 1) State 00 is reset
- 2) Output Z=1 only when the input sequence is 101, so this could be "101" pattern detector.
- 3) State "10" is referred to as "illegal state", "unused state" or an "unreachable state".
- 4) One way to ensure you don't end up in illegal state is to have a power on reset.

Use the PS/NS table or the composite K-map to obtain a state diagram to show the behavior of the circuit.


## An example VIII

 

## Note

Since we have two flip-flops, the state machine has 4 states.


# An example IX

 

Classic State machine

- \* Links show input, output in 1s and 0s
- \* State is inside the circles

## Legend

 

## Notes

- 1) State 00 is reset
- 2) Output Z=1 only when the input sequence is 101, so this could be "101" pattern detector.
- 3) State "10" is referred to as "illegal state", "unused state" or an "unreachable state".
- 4) One way to ensure you don't end up in illegal state is to have a power on reset.

# An example X

In the case of Moore machines, we put outputs inside the circle:


- They only depends on the current state

This constitutes a simplified State machine

It shows the links between states in Boolean expressions.
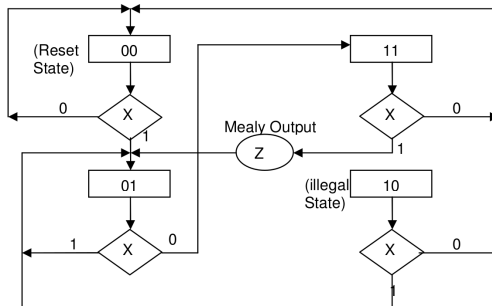
# An example XI

An Algorithmic State Machine (ASM) also describes the functionality:



Note: When Z is not shown, it is assumed the output is 0.

# References (Homework) I



Nelson, V. P., Nagle, H. T., Carroll, B. D., and Irwin, J. D.  
(1995).

*Digital logic circuit analysis and design.*

Prentice-Hall, Inc.