

Lab 1

Shane Sheehan
sheehas1@scss.tcd.ie

Semester II (2017)

1 Design an XOR using NAND gates

- Implement: $F(X, Y) = X \oplus Y$
 - Hint: Complement every input and output; Swap ORs and ANDs;
Seen before