

# **UNIVERSITY OF DUBLIN TRINITY COLLEGE**

**Faculty of Engineering, Mathematics and Science**

**School of Computer Science & Statistics**

**Integrated Computer Science Programme**

**Trinity Term 2014**

## **CS1026 – Digital Logic Design**

**Monday, 28<sup>th</sup> April 2014**

**Sports Centre**

**14:00 - 17:00**

**Prof. John Waldron and Dr. Eoin Creedon**

---

### **Instructions to Candidates**

**You must answer TWO questions from Section A and TWO questions from Section B.**

Please answer Section A and Section B in separate answer booklets.


Each question is worth 25 marks.

### **Permitted Materials**

Non-programmable calculators are permitted for this examination. Please indicate the make and model of your calculator on the front of your first answer book.

## Section A

 1. (a) Write down the truth table of an Exclusive OR gate. Draw the traditional symbol for an EOR gate. (5 marks)
  - (b) Draw a circuit diagram to show how an Exclusive OR gate can be constructed using only four NAND gates. (10 marks)
  - (c) Write down the truth table for a half adder and draw a circuit to implement it using an Exclusive OR gate and an AND gate. (10 marks)
2. (a) Write down the truth table of a NAND gate. Draw a circuit diagram showing a CMOS implementation of a 2-input NAND gate that uses four transistors. (5 marks)
  - (b) Write down a boolean expression for the circuit shown below. Using the theorems of boolean algebra find and draw the simplest circuit that implements the function Y. (10 marks)



(10 marks)

- (c) Find the minterms of the following boolean expression by first plotting it on a karnaugh map

$$wyz + w'x' + wxz' \quad (10 \text{ marks})$$

3. (a) Write down the truth table for a two to four line decoder with active low enable and active low outputs. (5 marks)
- (b) Draw a circuit to implement a two to four line decoder with active low enable and active low outputs using only inverters and NAND gates. (10 marks)
- (c) Draw a circuit that implements a full adder using only a decoder and external OR gates. (10 marks)

## Section B

1. (a) Explain *positively* edge triggered and *negatively* edge triggered flip-flops. (4 marks)  
(b) Explain the terms *setup time* and *hold time* in relation to flip-flops. (6 marks)  
(c) Discuss Algorithmic State Machines, including details on the symbols that make up a typical ASM diagram. (10 marks)  
(d) Describe and discuss *self starting* counters. (5 marks)
2. Using Quine-McCluskey create the minimal circuit which will identify if a user input number is a prime number or not, in the range 2 to 63. The circuit should output a 1 if the number is prime and a zero otherwise. Prime numbers are numbers which are divisible only by themselves or 1. **Use of any other method will attract no marks.** (25 marks)
3. (a) List the excitation table of a *JK* flip-flop. (5 marks)  
(b) Use *JK* flip-flops to design the logic for a synchronous counter that counts in the following sequence:  

0, 1, 3, 2, 6, 7, 5, 4

The counter should return to 0 after it reaches 4. Verify that the counter is self starting. (20 marks)