


LAB 1 WRITE UP

Title: CS1026 Lab 1 (XOR Gate)

Date: 26/10/2017

Aim: To design an XOR using NAND Gates to implement the function $F(a,b) = a'b + ab'$.

Logic Diagram:

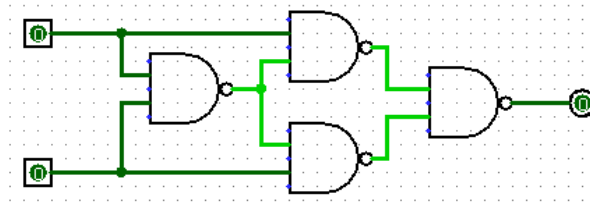

Analysis:

- I began by examining the truth table for an XOR gate with two inputs and found the variables needed to satisfy which are $x'y + xy'$
- Using Boolean algebra I expanded this function until I came upon a solution that contained parts which were in the form $(ab)'$
- I then designed a circuit to implement the Boolean algebra solution on the design software Logisim
- Following this I then tested the circuit using the input variables a and b to see if it was in fact an XOR Gate

Boolean Algebra:

$$F = a'b + ab'$$

$$= a'b + ab' + aa' + bb'$$

$$= (a+b)(a'+b') \text{ Simplifying}$$

$$= (a+b)(ab)' \text{ DeMorgans}$$

$$= a(ab)' + b(ab)'$$

$$F' = [a(ab)' + b(ab)']' \text{ Find } F'$$

$$= (a(ab)')' \cdot (b(ab)')' \text{ DeMorgans}$$

$$F = [(a(ab)')' \cdot (b(ab)')']' \text{ Invert to } F$$