

# CS1026 – Digital Logic Design

## Sequential Logic Analysis

Alistair Morris <sup>1</sup>

<sup>1</sup>Distributed Systems Group  
Trinity College Dublin

March 21, 2016

# Today's Overview

- 1 FSM – A quick recap
- 2 Example 1
- 3 Optional Homework.. :-O

# Synchronous Finite State Machine Design I

## Common Examples of Synchronous FSM

- Up and Down Binary Counters
- Shift Registers
- Sequence Detectors
- Controllers

# Synchronous Finite State Machine Design II

We use the:

- Seven-Step Design Process for Synchronous Sequential Design
- Also called *Classical Design*

# Synchronous Finite State Machine Design III

Organising the Design Specifications Use one or more of the following tools:

- Timing Diagram
- State Diagram
- ASM Chart

# Synchronous Finite State Machine Design IV

Determine the number of flip-flops based on the number of states

- You may use full encoding or *one-hot* encoding
- Full encoding utilise all possible combinations of the flip-flops

How many flip flops?

To decide the number of flip-flops we use the following inequality:  
 $2^n \geq \text{No. of States}$


# Synchronous Finite State Machine Design V

*One-hot* encoding  $\implies$  when the flip-flop has an output 1

Thus:

- The number of flip-flops = No. of States
- Once we know the number of flip-flops
  - Assign one variable for each of the flip-flop output

 
# Synchronous Finite State Machine Design VI



Classic State machine

- \* Links show input, output in 1s and 0s
- \* State is inside the circles

## Legend

 

## Notes

- 1) State 00 is reset
- 2) Output Z=1 only when the input sequence is 101, so this could be "101" pattern detector.
- 3) State "10" is referred to as "illegal state", "unused state" or an "unreachable state".
- 4) One way to ensure you don't end up in illegal state is to have a power on reset.

Assign a unique code to each state:

- A specific value for present state variables



# Synchronous Finite State Machine Design VII

Select the flip-flop type and draw the Present State/Next State (PS/NS) table:

Asynchronous Clear Input CLR'	Present State Y1 Y2		Next State Y1 <sup>+</sup> Y2 <sup>+</sup>		Present Output RCO
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1
0	X	X	0	0	0

**Present State / Next State (PS/NS) Table**

Present State Y1 Y2		Next State Y1 <sup>+</sup> Y2 <sup>+</sup>		Present Output RCO
0	0	0	1	0
0	1	1	0	0
1	0	1	1	0
1	1	0	0	1

**Simplified PS/NS Table**

(Note: CLR'=0 → Y1Y2=00)

- This determines the excitation input equations and the Moore and/or Mealy output equations.

# Synchronous Finite State Machine Design VIII

Remember the excitation input and next state relationship flip-flops:

- D flip-flops:  $D = Y^+$  or  $Y^+ = D$
- J-K flip-flops:  $J = Y^+$  or  $K = Y^{+'}$  or  $Y^+ = JY' + K'Y$
- T flip-flops:  $T = Y^+ \oplus Y$  or  $Y^+ = T \oplus Y$

# Synchronous Finite State Machine Design IX

The other *more practical* stages

- Draw the circuit schematic (paper or CAD tool).
- Perform a simulation to test the functionality of the design
- Implement the design with hardware


# Ripple Carry Output Counter [Nelson et al., 1995] I

## Our Task

- Design a 2-bit binary up-counter with a ripple carry output (*RCO*) using D flip-flops
- Note: The input  $\text{CLR}'$  denotes an asynchronous input that overrides the clock

# Ripple Carry Output Counter [Nelson et al., 1995] II

A timing diagram helps..

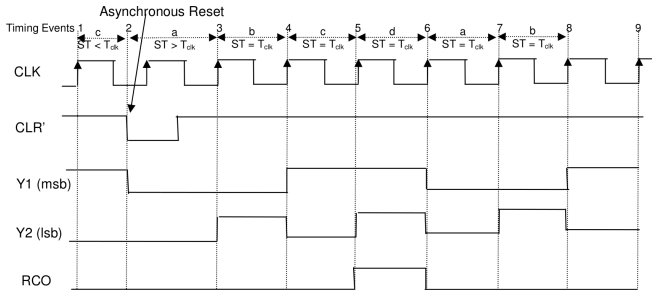


# Ripple Carry Output Counter [Nelson et al., 1995] III

A few things to remember:

- 1  $T_{clk}$  is the clock period and  $ST$  is the state time.
- 2 The first two events are less and then more than  $T_{clk}$ .
- 3  $Y1Y2$  are the states (counts).
- 4  $RCO$  is a Moore output indicating when the maximum count has been reached.
 
# Ripple Carry Output Counter [Nelson et al., 1995] IV

Although a timing diagram appears more complete, we can understand state diagram better:



- Since it does not contain the clock timing information.

# Ripple Carry Output Counter [Nelson et al., 1995] V

We can use a PS/NS table to describe the functionality (Step 1):

Asynchronous Clear Input CLR'	Present State		Next State		Present Output RCO
CLR'	Y1	Y2	Y1 <sup>+</sup>	Y2 <sup>+</sup>	RCO
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1
0	X	X	0	0	0

**Present State / Next State (PS/NS) Table**

Present State		Next State		Present Output RCO
Y1	Y2	Y1 <sup>+</sup>	Y2 <sup>+</sup>	RCO
0	0	0	1	0
0	1	1	0	0
1	0	1	1	0
1	1	0	0	1

**Simplified PS/NS Table**

(Note: CLR' = 0 → Y1Y2 = 00)

## Top hint

The *Next state*, *NS* defines the state of the machine

- During the next clock cycle



# Ripple Carry Output Counter [Nelson et al., 1995] VI

Step 2:

- Determine the no. of flip-flops based on the no. of states
- For full encoding – no. of states =  $4 \leq 2^2$

Step 3:

- Assign Unique code to each state
  - We already did this in the state diagram

# Ripple Carry Output Counter [Nelson et al., 1995] VII

Step 4:


- Write the excitation-input equations

Remember

The D flip-flop excitation equation:  $D = Y^+$

# Ripple Carry Output Counter [Nelson et al., 1995] VIII

More Step 4:

 

- The K-map for each of the desired outputs:  $Y1^+$ ,  $Y2^+$ ,  $RCO$  helps us determine excitation-input equations

# Ripple Carry Output Counter [Nelson et al., 1995] IX

Last bit of step 4:


Y1Y2 \	Y1 <sup>+</sup>	Y2 <sup>+</sup>	RCO
00	0	1	0
01	1	0	0
11	0	0	1
10	1	1	0

A composite K-map is a short hand for multiple K-maps.

- Draw a composite K-map for each of the desired outputs:
  - Y1, Y2, RCO

# Ripple Carry Output Counter [Nelson et al., 1995] X

Now relax.. (Step 5)

 

■ Draw the Circuit Schematic

# Ripple Carry Output Counter [Nelson et al., 1995] XI

We skip steps 6 and 7

- Remember to do them for labs
- And note them when doing exams
  - It shows understanding!

# Some for you to try

## Example Style Question

Design a synchronous sequential circuit called *Div-by-3* having an output  $Z$  that divides the system clock frequency  $f$  CLK by 3.

- Use an output duty cycle of two-thirds
  - 2 CLK cycle high, 1 cycle low
- Design the circuit using positive-edge-triggered flip-flops

# References (Homework) I



Nelson, V. P., Nagle, H. T., Carroll, B. D., and Irwin, J. D.  
(1995).

*Digital logic circuit analysis and design.*

Prentice-Hall, Inc.