

CS1026 Lab 3

Design, build and test a circuit that uses a 74138 3 to 8-line decoder/demultiplexer and minimal additional circuitry to implement the function

$$F = x'yz' + xz$$